






### Make the LED blink



### Wire the LED

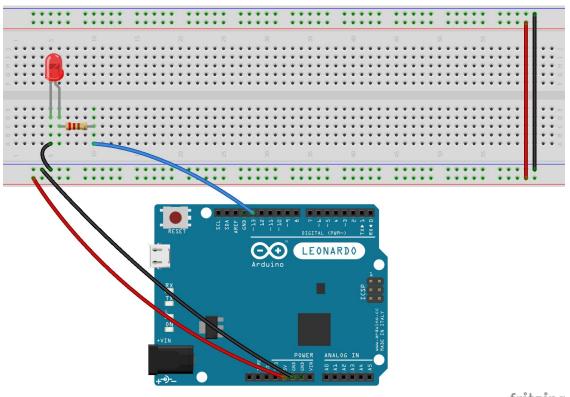


fritzing

## Control the brightness of the LED




#### **Pulse Width Modulation**

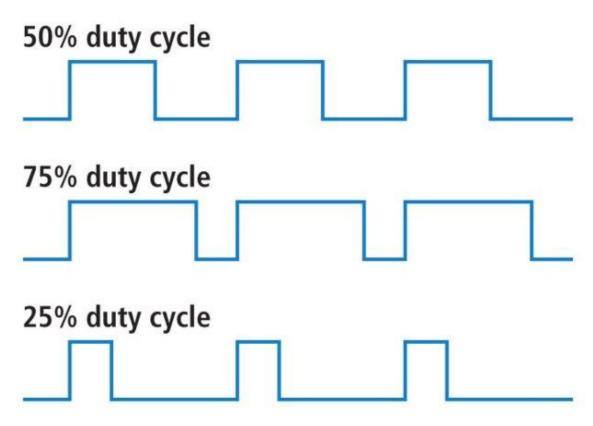

#### Press button to turn on LED



## Wire push button

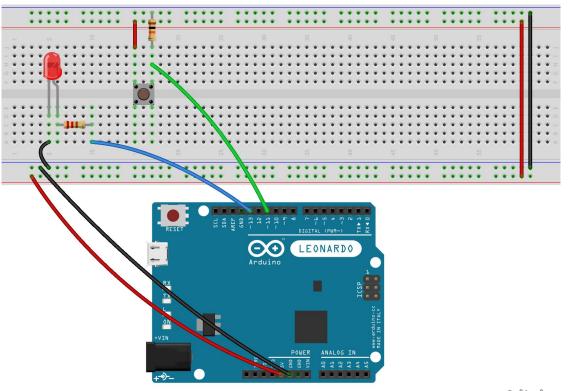


fritzing

## Press button to toggle LED state




## Debouncing

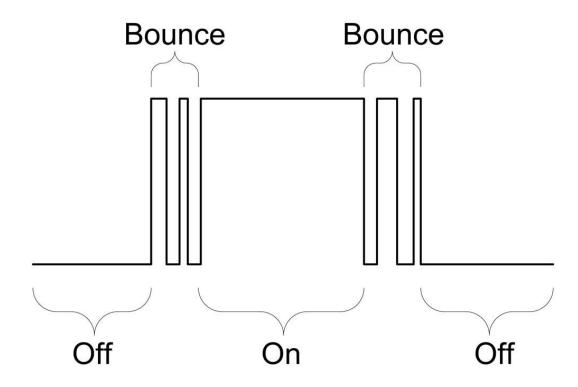


## Control the brightness of the LED with pot




## Wire the potentiometer

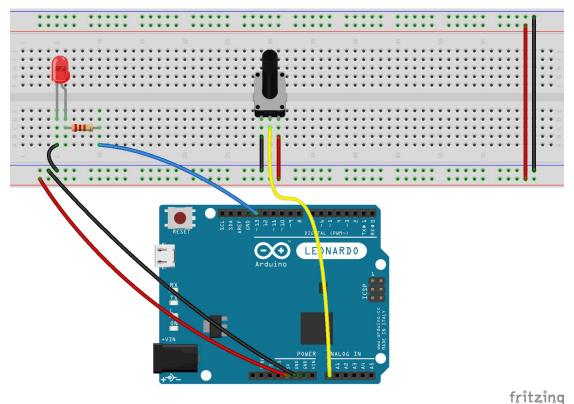
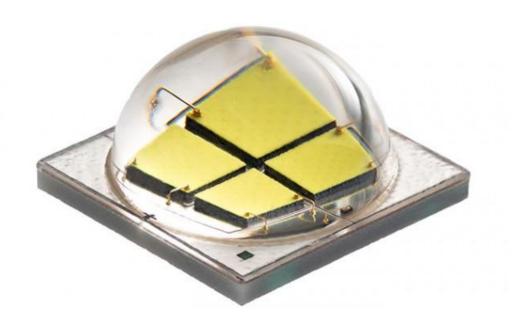
## Control the brightness of the LED with light



## Wire the light dependent resistor

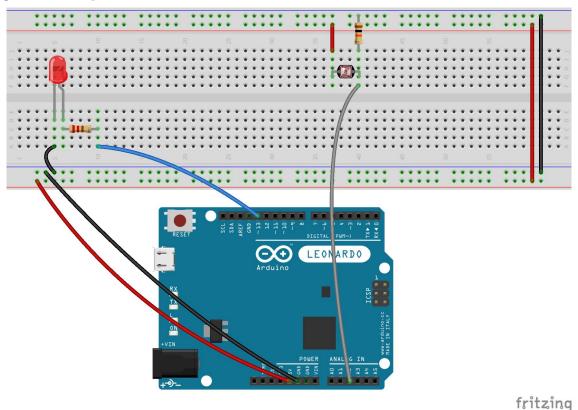


### **Download Capacitive Sense Library**

```
$ cd ~/Documents/Arduino/libraries
$ git clone git@github.com:arduino-libraries/CapacitiveSensor.git
```

Toggle the LED by touching



#### Wire the touch sensor

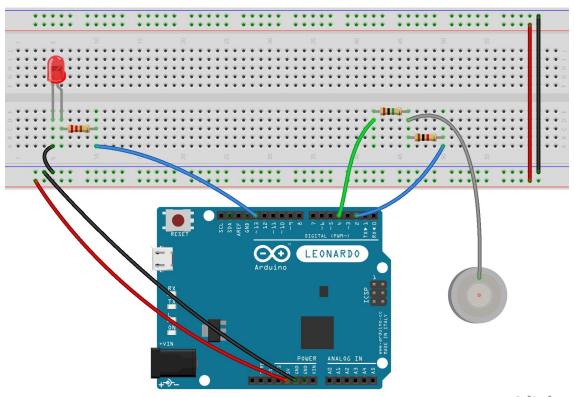

fritzing